

INSTRUCTION MANUAL

Advanced Physics Lab

Electronics A+D

Modern Aspect of Data Taking and Processing with a Microcontroller

Pirmin Berger & Michael Reichmann

Abstract

The experiment “Digital Electronic” provides an introduction into modern data taking by operating simple digital circuits utilising an Arduino board. This manual will inform you about the Arduino board, the installation of the required software and the electrical components you will have to use. Basic knowledge on electronics, how to use oscilloscopes, bread boards and power supplies is recommended.

During the experiment you will learn how to build a circuit that measures the temperature, how to operate it using the Arduino board and to modify and improve it using more components.

In case you should already have previous knowledge we will provide many more material and own ideas on implementation are very welcome and can be built consulting the assistants.

Contents

1	Introduction	1
1.1	Arduino Board	1
1.2	Transistor	1
2	Basics	3
2.1	Arduino Uno	3
2.2	Grove Base Shield	4
2.3	The Software	4
2.3.1	Arduino integrated development environment (IDE)	4
2.3.2	Board Drivers	5
2.4	Programming	5
2.5	Project Management with	7
2.6	Voltage Divider	7
2.7	Thermistor	7
2.8	Temperature Sensor	8
2.9	Bipolar Junction Transistor	8
2.9.1	Working Principle	8
2.9.2	Common Collector	9
2.10	Operational Amplifier	10
2.11	PID Controller	10
3	Setup and Experimental Procedure	10
3.1	Experimental Material	10
3.2	Setting up the Arduino	11
3.2.1	Software installation	11
3.2.2	Connect the Arduino	11
3.2.3	Your First Sketch	12
3.3	Blinking LED on Bread Board	12
3.4	Grove Temperature Sensor	12
3.5	Grove Display and Potentiometer	13
3.6	Data Handling	14
3.7	Building Your Own Temperature Sensor	14
3.8	Building a Heating System	15
3.9	Building a Cooling System	15
3.10	Read Out the Fan Speed	16
3.11	Building a PID Controller (Advanced)	16
4	Analysis / Protocol	16

1 Introduction

Arduino is a computer company, project and user community based on easy-to-use hardware and software, that designs and manufactures single-board microcontrollers and microcontroller kits for building digital devices and interactive objects that can sense and control objects in the physical and digital world. All products are distributed as open-source hardware and software, and it's licences permit the manufacture of Arduino boards and software distribution by anyone. The boards are commercially available in preassembled form, or as do-it-yourself (DIY) kits.

The Arduino project started in 2003 as a program for students without a background in electronics and programming at the Interaction Design Institute in Ivrea (Italy). The aim was to provide a low-cost and easy way for novices and professionals to create devices that interact with their environment using sensors and actuators. The actual name Arduino comes from a bar in Ivrea, where some of the founders of the project used to meet. The bar was named after Arduin of Ivrea, who was the margrave of the March of Ivrea and King of Italy from 1002 to 1014 [?].

In order to work with the Arduino Boards the Arduino programming language, based on Wiring, and the Arduino Software (IDE), based on the Processing are used [?]. Both Wiring and Processing are programming languages using a simplified dialect of features from the programming languages C and C++.

1.1 Arduino Board

The original boards were produced by the Italian company Smart Projects but as of 2018, 22 versions of the Arduino hardware have been commercially produced. The information and specifications of these boards can be found on this [website](#). During this Lab you will work the Arduino Uno shown in Figure 1.

The Arduino Boards use a variety of microprocessors and controllers and are equipped with sets of digital and analogue input/output (I/O) pins that may be interfaced to various expansion boards or Breadboards (shields) and other circuits. The boards feature serial communications interfaces, Universal Serial Bus (USB) on some models, which are also used for loading programs from personal computers.

Arduino boards are able to read inputs - light on a sensor, a finger on a button, or a Twitter message - and turn it into an output - activating a motor, turning on an LED, publishing something online. You can tell the board what to do by sending a set of instructions to the microcontroller.

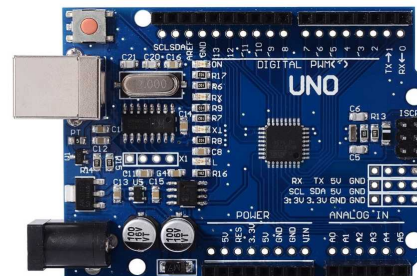


Figure 1: Arduino Uno.

1.2 Transistor

The invention of the transistor was announced in 1948 by the American physicists, J. Bardeen and W. H. Brattain as a new type of amplifying device made from semiconducting crystals. At that time almost no one could have foreseen the revolutionary developments that were to follow, developments so important and far-reaching as to change the whole outlook of the

science and technology of electronics. The physical principles of a transistor had been worked out in conjunction with their colleague, W. Shockley. In recognition of their work the three physicists were awarded jointly the Nobel Prize for Physics in 1956.



(a) Point-contact transistor.



(b) Bardeen, Brattain and Shockley.

The term “transistor” is a combination from the words *transformer* and *resistor*, since the device is made from resistor material and transformer action is involved in the operation. In the beginning only point-contact transistors existed, but due to their vulnerability to mechanical shock they were soon replaced by junction transistors which are firmly established now [?].

The transistor is the key active component in practically all modern electronics. It is considered as one of the greatest inventions of the 20th century. Its importance in today’s society rests on its ability to be mass-produced using a highly automated process that achieves astonishingly low per-transistor costs (10 femto\$/transistor) [?].


Although billions of individually packaged (discrete) transistors are produced every year the vast majority of transistors are now produced in integrated circuits (ICs). A logic gate consists of up to about twenty transistors whereas an advanced microprocessor, as of 2009, can use as many as 3 billion transistors. In 2014, about 10 billion transistors were built for each single person on Earth [?].

The working principle of the transistor will be covered in subsection 2.9.

2 Basics

This section will give you the basic information about the components we are using in this lab.

2.1 Arduino Uno

 

1. **Digital pins:** used with `digitalWrite()`, `digitalRead()`, and `analogWrite()` methods, only works on pins with the pulse width modulation (PWM) symbol
2. **Pin 13 LED:** only built-in actuator
3. **Power LED**
4. **ATmega microcontroller**
5. **Analogue in:** used with `analogRead()` method
6. **GND and 5V pins:** provide 5 V power and ground (GND) to the circuits
7. **Power connector:** additional power supply, accepted voltages: 7 ~ 12 V
8. **TX and RX LEDs:** indicate communication between Arduino and computer
9. **USB port:** used for powering and communication with computer
10. **Reset button:** resets the ATmega microcontroller

2.2 Grove Base Shield

The so called shields are printed circuit expansion boards, which plug into the normally supplied Arduino pin headers. The Grove Base Shield is one example that simplifies projects that require a lot of sensors or LEDs. With the Grove connectors on the base board, one can add all the Grove modules to the Arduino Uno very conveniently.

 


Figure 3: Grove shield.

There are 16 Grove connectors on the Base Shield which are shown in Table 1. Apart from the connectors the board also consists of a reset (RST) button, a green LED to indicating power status, a toggle switch and four rows of pinouts, which is equivalent to the pinout of the Arduino.

Specification	Name	Quantity
Analog	A0/A1/A2/A3	4
Digital	D2/D3/D4/D5/D6/D7/D8	7
UART	UART	1
I2C	I2C	4

Table 1: Base Shield connectors.

Every Grove connector has four wires, one of which is the voltage common collector (VCC). Since some micro-controller main boards need need different supply voltages the power toggle switch allows you to select the suitable voltage. In the case of the Arduino Uno a voltage of 5 V is required [?].

2.3 The Software

2.3.1 Arduino IDE

All you require to write programs and upload them to your board is the Arduino Software (IDE). There are two options how to use it:

1. Online IDE

- no installation required
 - needs plugin if you want to upload sketches from Linux
- requires you to create account with e-mail verification
- save sketches in cloud (available from all devices)
- always most up-to-date version
- instructions on the website

2. Desktop IDE

- if you want to work offline
- installation usually very straightforward and in has general no dependencies
- if you need help, follow installation instructions depending on your operating system (OS)
 - [Linux](#)
 - [Mac OS X](#)
 - [Windows](#)

2.3.2 Board Drivers

First the Arduino board has to be connected to the computer via the USB cable which will power the board indicated by the green power (PWR) LED. The board drivers should then install automatically in Linux, Mac OS X and Windows. If the board was not properly recognised, follow these [instructions](#).

2.4 Programming

In order to get a feeling for the programming language it is recommended to have a look at the examples first which can be found under: **File > Examples**

A list of the most common methods is shown in Table 2. For more information look at the [detailed description](#).

Category	Method Syntax	Description
Sketch		called once at the start of the sketch, used to initialise variables, pin modes, etc.
		loops consecutively after setup was called
Digital I/O		reads the value from the digital pin (HIGH or LOW)
		writes HIGH or LOW value to the digital pin
		configures the pin as INPUT or OUTPUT
Analogue I/O		reads the value (0-1023) from the pin
		writes an analogue value (PWM wave) to the pin
		configures the reference voltage used for analogue input
Advanced I/O		generates a square wave of frequency f [Hz] for a duration [ms]
		returns the time [ms] of a pulse, if value is HIGH: waits until HIGH and stops when LOW
Time		pauses the program for a time [ms]
		returns time since starting the program [μ s]
		returns time since starting the program [ms]
Math		constrains a number x to be in range [a, b]
		re-maps x from range [a, b] to range [c, d]
		returns pseudo-random number in range [a, b]
		return the absolute value
	\vdots	further general math commands
Serial		initialise serial communication at speed [bit/s]
		prints the value to the serial port
		prints the value to the serial port with $[\backslash r \backslash n]$
		reads incoming serial data

Table 2: Most common methods for controlling the Arduino board and performing computations.

2.5 Project Management with git

Git is a version control system for tracking changes in computer files and coordinating work on those files among multiple people. It is primarily used for source code management in software development, but it can be used to keep track of changes in any set of files [?].

2.6 Voltage Divider

A voltage divider is a passive linear circuit that produces an output voltage V_{out} that is a fraction of its input voltage V_{in} . Voltage division is the result of distributing the input voltage among the components of the divider. A simple example of a voltage divider is two resistors connected in series, with V_{in} across the resistor pair and V_{out} emerging from the connection between them as shown in Figure 4.

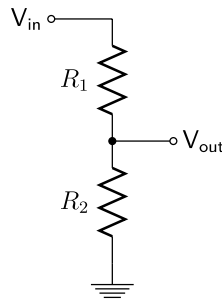


Figure 4: Voltage divider.

Resistor voltage dividers are commonly used to create reference voltages, or to reduce the magnitude of a voltage so it can be measured. Using Ohm's law one can easily derive the formula for V_{out} :

$$V_{\text{out}} = \frac{R_2}{R_1 + R_2} \cdot V_{\text{in}} \quad (1)$$

2.7 Thermistor

If, for a given temperature, the current is directly proportional to the applied voltage the electrical component is said to obey Ohm's law. Such components are called linear resistors. If a component does not meet this requirement it is termed a non-linear resistor, which falls into two classes – the temperature-sensitive type and the voltage-sensitive type. The temperature-sensitive types are often known as thermistors and change the resistance very reproducibly. The word is a portmanteau of *THERM*ally-sensitive and resIStOR.

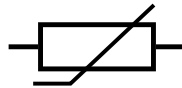


Figure 5: Electronic symbol of the thermistor

They consist of the sintered oxides of manganese and nickel with small amounts of copper, cobalt or iron added to vary the properties and the physical shape is usually a bead, rod or

a disc. The electronic symbol is shown in Figure 5. The resistance is given by

$$R = R_0 \cdot e^{-B\left(\frac{1}{T_0} - \frac{1}{T}\right)} \quad (2)$$

where B is a constant depending upon the composition and physical size, T is the temperature in °K, and R_0 the resistance at ambient room temperature T_0 ($25^\circ\text{C} = 298.15\text{ K}$). Thermistors can be classified into two types, depending on the classification of B . If B is positive, the resistance increases with increasing temperature, and the device is called a positive temperature coefficient (PTC) thermistor, or posistor. If B is negative, the resistance decreases with increasing temperature, and the device is called a negative temperature coefficient (NTC) thermistor.

2.8 Temperature Sensor

Thermistors have very widespread applications as thermometers. We know that a NTC thermistor varies its resistance as a function of the temperature, but resistance is not the easiest parameter to measure. In our case we want to feed a signal into an analogue-to-digital converter (ADC) to treat it numerically and compute the actual temperature. Now, the ADC of the Arduino requires a voltage at its input.

An easy solution is to install the NTC in a voltage divider as shown in subsection 2.6. It requires only one additional fixed resistor R_0 . V_{in} is the reference voltage used of the ADC and V_{out} the measured voltage. So what you will measure in the end is just a digital 10 bit value corresponding to the divided voltage where the maximum of $2^{10} - 1 = 1023$ corresponds to V_{in} . In order to convert it into the resistance of the thermistor we have to use Equation 1:

$$R = \left(\frac{V_{\text{in}}}{V_{\text{out}}} - 1\right) \cdot R_0 = \left(\frac{1023}{V_{\text{meas}}} - 1\right) \cdot R_0 \quad (3)$$

Now we need to convert the resistance into the temperature using Equation 2:

$$\frac{1}{T} = \frac{\ln\left(\frac{R}{R_0}\right)}{B} + \frac{1}{T_0} \quad (4)$$

Note that this temperature will be in Kelvin!

2.9 Bipolar Junction Transistor

A bipolar junction transistor (BJT) is a type of transistor that uses both electron and hole charge carriers. For their operation, BJTs use two junctions between two semiconductor types, n-type and p-type and thus can be manufactured in two types, NPN and PNP. The basic function of a BJT is to amplify current which allows it to be used as amplifiers or switches, giving them wide applicability in electronic equipment.

2.9.1 Working Principle

Since a transistor consists of two pn junctions within a single crystal, transistor action can be explained with Figure 8. For diagrammatic purposes the base region is shown fairly thick,

but in fact the pn junctions are very closely spaced and the active portion of the base is very thin.

The charge flow in a BJT is due to diffusion of charge carriers across a junction between two regions of different charge concentrations. The regions of a BJT are called emitter, collector, and base. Typically, the emitter region is heavily doped compared to the other two layers, whereas the majority charge carrier concentrations in base and collector layers are about the same.

In the absence of any external applied voltages the collector and emitter depletion layers are about the same thickness, the widths depending upon the relative doping of the collector, emitter and base regions. During normal transistor operation the emitter-base junction is forward biased so that current flows easily in the input or signal circuit. The bias voltage V_{BE} is about 200 mV for germanium transistors and about 400 mV for silicon devices. The collector-base junction is reverse-biased by the main supply voltage V_{CB} typically with 4.5 V, 6 V and 9 V. The collector junction is therefore heavily reversed-biased and the depletion layer there is quite thick.

The injection of a hole into the base region by a signal source will now be considered. Once in the base, the hole attracts an electron from the emitter region. The recombination of the hole and electron is not likely to occur however, since the base region is lightly doped compared with the emitter region and so the lifetime of the electron in the base region is quite long. In addition the base is extremely thin so the electron, instead of combining with the signal hole or with a hole of the p-type base material, diffuses into the collector-base junction. The electron then comes under the influence of the strong field there and is swept into the collector and hence into the load circuit. In a good transistor many electrons pass into the collector region before eventually the signal hole is eliminated by combination with an electron. A small signal current can thus give rise to a large load current i_C , and so current amplification has taken place. In practical transistors for every hole injected into the base 50 to 250 electrons may be influenced to flow into the collector region. The current gain or amplification is therefore 50 to 250. It is usually given by the symbol β .

An PNP transistor behaves in a similar fashion except that electrons are injected into the base and holes flow from the emitter into the collector. To maintain the correct bias conditions the polarity of the external voltages must be reversed.

Figure 9 shows the three basic transistor arrangements. The common emitter mode is the most commonly used arrangement for voltage amplification because very little current is required from the signal source.

The common base mode of operation is also capable of voltage amplification. This is achieved by the use of high values of load resistor. The transistor is able to maintain the current through the load because the device is a good constant current generator [?].

2.9.2 Common Collector

The common collector circuit shown in Figure 9c has a voltage gain of a little less than unity and so is useless as a voltage amplifier. However this circuit has very important impedance matching properties and is typically used as a voltage buffer. In this circuit the base serves as the input, the emitter is the output, and the collector is common to both.

The voltage gain is just a little less than one since the emitter voltage is constrained at the voltage drop over the diode of about 0.6 V (for silicon) below the base. The transistor

continuously monitors V_D and adjusts its emitter voltage almost equal (less V_{BE0}) to the input voltage by passing the according collector current through the emitter resistor R_E . As a result, the output voltage follows the input voltage variations from V_{BE0} up to V_+ ; hence also the name, emitter follower. This circuit is useful because it has a large input impedance, so it will not load down the previous circuit and a small output impedance, so it can drive low-resistance loads

2.10 Operational Amplifier

Should be covered in AP next semester

2.11 PID Controller

A proportional–integral–derivative (PID) controller is a control loop feedback mechanism widely used in industrial control systems and a variety of other applications requiring continuously modulated control. A PID controller continuously calculates an error value et as the difference between a desired setpoint (SP) and a measured process variable (PV) and applies a correction based on proportional, integral, and derivative terms (denoted P, I, and D respectively) which give the controller its name.

In practical terms it automatically applies accurate and responsive correction to a control function. An everyday example is the cruise control on a road vehicle; where external influences such as gradients would cause speed changes, and the driver has the ability to alter the desired set speed. The PID algorithm restores the actual speed to the desired speed in the optimum way, without delay or overshoot, by controlling the power output of the vehicle's engine [?].

3 Setup and Experimental Procedure

The Digital Electronics Lab is meant to be very open in implementation. The aim will be to build an automated cooling system. We will guide you through this process step by step, but you are also encouraged to bring in your own ideas of other possible implementations!

3.1 Experimental Material

You will find the following objects on your test stand:

- 1 Arduino Uno Board
- 1 Oscilloscope
- 2 Probes
- 1 Multimeter
- 1 USB Type B cable
- 1 Breadboard
- 1 Grove Starter Kit for Arduino

- 1 Base Shield
 - 1 LCD RGB Backlight
 - 1 Smart Relay
 - 1 Buzzer
 - 1 Sound Sensor
 - 1 Touch Sensor
 - 1 Rotary Angle Sensor
 - 1 Temperature Sensor
 - 1 LED Module
 - 3 Dip LEDs (red, green, blue)
 - 1 Light Sensor
 - 1 Button
 - 1 Mini Servo
 - 10 Grove Cables
- 1 3-pin fan
 - 1 operational amplifier ([LM358](#))
 - 1 NPN transistor ([BC547](#))
 - 1 NTC thermistor ([B57164-K104-J](#))

In addition you should bring a lab book to note down everything what you do and measure (immediately after the execution). Please write clearly and meticulously since it will greatly help you to find mistakes and to write your report!

3.2 Setting up the Arduino

3.2.1 Software installation

We highly recommend you to install the Arduino IDE on your machine so that you can access it any time. If you should have trouble with the installation or would prefer to work you can also use the online IDE.

- install IDE following subsection 2.3 (Do we provide some laptops just in case?)

3.2.2 Connect the Arduino

- connect the Arduino to your computer and check if it is recognised by the IDE
 - select the correct port: **Tools > Port**
 - get board info: **Tools > Get Board Info**

3.2.3 Your First Sketch

- create your sketch directory
 - you can link it to your IDE: **File > Preferences > Sketchbook Location**
- create a git repository for this project in the sketch folder
- write a sketch that turns on the built in LED
 - name it `LedOn.ino`
 -

3.3 Blinking LED on Bread Board

This task will teach you how to use the Breadboard with the Arduino and the difference between `pinMode` and `digitalWrite`.

- supply the Breadboard with 5 V from the Arduino
- connect a LED to the Breadboard
- write a sketch (`Blink.ino`) that makes the LED blink with a frequency of 10 Hz using the `digitalWrite` method
- connect a second LED to the circuit
- write a sketch (`Blink2.ino`) that makes the second LED blink in a different pattern than the first one
 - why is `pinMode` not working anymore?
 - use a timer with `delay` or `millis`

3.4 Grove Temperature Sensor

In this experiment you will work with the [Grove - Temperature Sensor V1.2](#). It uses a NTC thermistor to detect the ambient temperature. The specifications are shown in Table 3.

Specification	Value
Operating voltage	3.3 ~ 5.0 V
Zero power resistance	$(100 \pm 1) \text{ k}\Omega$
Operating temperature range	$-40 \sim +125 \text{ }^{\circ}\text{C}$
Nominal B -constant	4250 ~ 4299 K

Table 3: Grove-Temperature Sensor V1.2 specifications.

- connect the Grove Base Shield to your Arduino
- connect the Grove Temperature Sensor to the shield

- think about which connector to choose on the shield
 - ?
- write a sketch (`GroveTemp.ino`) that measures the ambient temperature
 - read the voltage value from the sensor
 - convert the voltage into the corresponding resistance
 - convert the resistance into a temperature in °C
 - write the temperature to the serial interface
 - look at the data with the Arduino Serial Monitor:
`Tools > Serial Monitor ()`
 - look at the data with the Arduino Serial Plotter:
`Tools > Serial Plotter ()`

3.5 Grove Display and Potentiometer

As a next step, we will add two more components from the Grove kit: a display to output the current temperature read by the sensor and a potentiometer to set the threshold for our two-point temperature control later.

- add the display to your project
 - install the libraries from http://wiki.seeedstudio.com/Grove-LCD_RGB_Backlight/
 - look at the example code on the above website, especially on how to include the libraries in your project and how to initialize it during the `setup()!` (`setup()!`) routine
 - make sure the "3V3V_{CC5V}" switch on the Grove shield is set to 5V, otherwise the display will not work correctly
- modify your project such that the measured temperature is printed on the display every second
- define a fixed threshold in your code, e.g. 30 degrees above which a LED is turned on. (As alternative you can change the background color of your display). Test if your project is working.
- now we want to make the threshold controllable without recompiling our project. For this purpose, connect the potentiometer (Grove Rotary Angle Sensor) to the Grove shield.
 - read the description at http://wiki.seeedstudio.com/Grove-Rotary_Angle_Sensor/
 - read-out the sensor with `analogRead()!` (`analogRead()!`)
 - to map the ADCs which range from 0 to 1023 to a reasonable temperature range (a, b), e.g. 20 to 40 degrees, the function `map(degrees, 0, 1023, a, b)!` (`map(degrees, 0, 1023, a, b)!`) can be used for convenience
- indicate the status below/above threshold also in the output to the serial interface, e.g. add a second number (0 = below threshold, 50 = above threshold) separated by a space
- test your code by varying the threshold below/above the room temperature

- the serial plotter should now draw a second line indicating whether below or above threshold
- optional: while turning the potentiometer, you can also print the threshold temperature on the display in the second row below the measured temperature

3.6 Data Handling

Even though one can use the Arduino IDE to look at the values from the temperature sensor, there is no way to save them. That is why we encourage you to write a short program to save the data to file so that you can use it afterwards. We recommend you to use python for this purpose, but feel free to use whatever you have the most experience with.

Once a sketch is uploaded to the microprocessor the Arduino will perform the loop until it is disconnected from power or overwritten by a new sketch. In order to read the data externally from the serial port you have to close the Arduino serial tools.

Example code in python:

- open the serial port
 -
 -
 - you can find the name of the port in the Arduino IDE
 - read a single line using the serial method
- print the line in the terminal using **print!** (**print!**)
- write the data to a text file (**data.txt**), every value on a single line
 - if you have trouble handling files in python follow this [guide](#)
- your program should repeat this until you terminate it e.g. by pressing CTRL+C.

Optional: If you use Linux or Mac, try to do all of the above with a single line of bash with less than 100 characters. Look at **read!** (**read!**) and **tee!** (**tee!**) commands.

3.7 Building Your Own Temperature Sensor

In this task you will build your own temperature sensor using discrete components. The [B57164-K104-J](#) thermistor has the specifications listed in Table 4.

Specification	Value
Operating voltage	3.3 ~ 5.0 V
Zero power resistance	(100 ± 5) kΩ
Operating temperature range	−55 ~ +125 °C
Nominal <i>B</i> -constant	(4600 ± 1340) K

Table 4: B57164-K104-J specifications.

- build a voltage divider circuit to convert the resistance into a measurable voltage
- use the operational amplifier to increase the outgoing signal
- reproduce the temperature measurements from subsection 3.5

3.8 Building a Heating System

Since it is boring to measure a constant temperature you build a system to heat your temperature sensor.

- connect a resistor (or a series of resistors) to the Breadboard
- calculate the power dissipation of the resistor
- heat the temperature sensor with the heater
- monitor the temperature
- measure time constant of the temperature rise?

3.9 Building a Cooling System

Many electrical components will produce heat under load and may break at critical temperatures. That is why many of complex systems like computers require cooling. You will now build a system that controls a fan and can regulate it's rotation speed.

- connect the fan to the breadboard, for the 4 pin header, the following conventions are used:
 - black: ground
 - yellow: 5V
 - green: tachometer read-out (will be used later)
 - blue: PWM control
- keep in mind that only a few of the digital pins (marked by "D" on the board) are able to use PWM, e.g. use digital pin 11

Now we can finally build the full two-point controller.

- define a low and high threshold, e.g. use the potentiometer for the high threshold and set the lower threshold a few degrees lower than the high one.
- set the duty cycle of the fan to 100% when above the high threshold
- set the duty cycle of the fan to 0% when below the low threshold
- setting the PWM duty-cycle can be done using the `analogWrite()` function
- if thresholds are set reasonably, you will see an oscillatory behavior. **Create a plot of temperature vs. time which shows multiple periods.**

3.10 Read Out the Fan Speed

We now want to use the built-in Hall Effect Sensor (HES) of the fan to measure its rotation speed. In every rotation this sensor will produce two pulses we can count and then convert to revolutions per minute (**RPM**). The maximum (for 100% duty cycle) according to the datasheet is 1900 RPM, with a tolerance of 10%, the minimum is around 230 RPM.

- calculate a rough estimate for the minimum frequency needed for reading the voltage on the tacho pin and be able to count the pulses? (Use Nyquist theorem) In practice, a much higher frequency should be used than the limit calculated above
- check the Arduino reference of **analogRead()** for the maximum frequency. Since we also have to do other work in the **loop()** function, the frequency should be also much less than the maximum. Make a reasonable choice.
- what is the expected uncertainty on the minimum and maximum RPM if we count pulses for 1 second?
- connect the tacho (green wire) of the fan to an analog pin of the Arduino, using a 10k pull-up resistor. (optional: figure out how to use internal pull-up resistor of the Arduino instead of a discrete component)
- what is the role of the pull-up resistor?
- count the pulses of the HES and convert the result to RPM. Is it within the range expected by the datasheet numbers?
- write the revolutions per minute (RPM) value to the serial output

3.11 Final measurements

Now that our device has all basic functionalities, we can perform some measurements with it.

- plot the fan RPM vs. the duty cycle. Which is the minimum duty cycle from which on the fan starts to spin?
- plot the equilibrium temperature vs. the duty cycle and the equilibrium temperature vs. the fan RPM

Scanning the points for the different duty cycles should be done without flashing the device in between. Instead the measurement programme (e.g. number of steps, seconds per step etc.) should be programmed into the Arduino.

3.12 Bi-directional communication with the computer (Advanced)

Until now we only read values from the device, but we can also write commands from the computer to the Arduino using the serial interface.

- instead of using the potentiometer to set the threshold, implement a way to set the threshold via serial commands

- one can use the SCPI protocol as a reference, e.g. set the threshold to 32 degrees with the command "SET:THR 32"
- which other commands are necessary to run the measurements from above section without hardcoding the measurement programme (e.g. number of steps, seconds per step etc.)?
- write a Python script to perform the measurements from above section via sending SCPI style commands to the Arduino

3.13 Building a PID Controller (Advanced)

To prevent your resistor from overheating you will now implement a PID controller to regulate it's temperature.

- build a setup including the heater and the fan
- measure the temperature of the resistor with your sensor
- write a sketch (`TControl.ino`) that uses PID to regulate the temperature of the resistor to a stable value

4 Analysis / Protocol

The analysis and the following protocol should be done such that the reader is able to reconstruct the described circuit and is able to proof that it is working correctly. That includes besides the exact description of all the used parts:

- A link to the repository with all the used sketches. The code should be written in a readable fashion according to [C++ coding guidelines](#) with meaningful denotations and sufficient comments.
- Circuit diagrams of **ALL** circuits. A circuit diagram consists of international standardised symbols for all parts in the circuit.

Besides you should answer all questions posed in section 3 describing the approach. Do not forget the results and a conclusion!

List of Figures

1	Arduino Uno.	1
3	Grove shield.	4
4	Voltage divider.	7
5	Electronic symbol of the thermistor	7
6	Resistance/temperature characteristic of a NTC thermistor.	III
7	Electronic symbols of the BJT.	IV
8	Diagrammatic representation of the amplifying action of a transistor.	IV
9	The three basic amplifier arrangements.	IV

List of Tables

1	Base Shield connectors.	4
2	Most common methods for controlling the Arduino board and performing computations.	6
3	Grove-Temperature Sensor V1.2 specifications.	12
4	B57164-K104-J specifications.	14

List of Acronyms

IDE integrated development environment

DIY do-it-yourself

USB Universal Serial Bus

I/O input/output

GND ground

RST reset

PWR power

IC integrated circuit

VCC voltage common collector

OS operating system

PTC positive temperature coefficient

NTC negative temperature coefficient

ADC analogue-to-digital converter

BJT bipolar junction transistor

PWM pulse width modulation

PID proportional–integral–derivative

RPM revolutions per minute

 


Figure 6: Resistance/temperature characteristic of a NTC thermistor.



Figure 7: Electronic symbols of the BJT.

 


Figure 8: Diagrammatic representation of the amplifying action of a transistor.

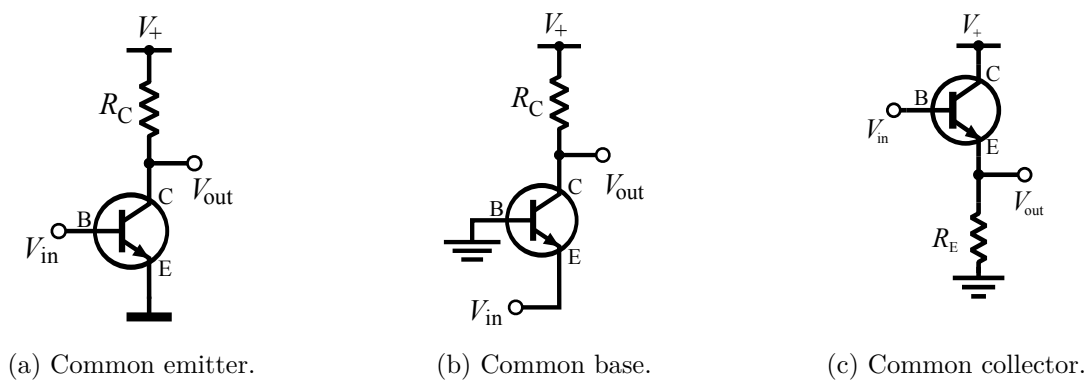


Figure 9: The three basic amplifier arrangements.